

Interfacing to AC Power Lines

Author: *Doug Cox*
Microchip Technology Inc.

INTRODUCTION

This application note describes a simple method for measuring parameters from the AC power line. Parameters such as zero crossing, frequency, and relative phase can be measured. This method is useful for measurements on 50, 60, and 400 Hz power systems with voltages up to several hundred volts. The method requires only one external component, a resistor, and is more reliable than previously published methods using capacitors or bulky, expensive transformers.


APPLICATIONS

This measurement method can be used in any application where power line parameters are used for system measurements or control. Typical applications are; switch timing (what part of the power cycle should the system be activated), power factor correction, power measurement, and power line monitor. An additional application is to generate timing or clock functions using the relatively stable power line frequency. This method is also useful for calibrating oscillator frequency for accurate timing measurements when an inaccurate reference such as an RC oscillator is used to clock the PIC16C5X.

THEORY OF OPERATION


This application takes advantage of the input static protection circuitry that exists on all I/O pins of a CMOS PIC16C5X. These protection circuits are designed to short the inputs to the power supplies when a large overvoltage is applied, thus protecting the chip from static electricity spikes. On PIC16C5X microcontrollers, this protection circuit is two large P-N diodes on each input (Figure 1). These diodes will short any voltage higher than VDD to the VDD supply and any voltage less than VSS to the VSS supply. They can take several milliamps of current without any damage to the chip. High voltages can be applied directly to the chip inputs as long as they are current limited.

FIGURE 1: PIC16C5X SERIES INPUT PROTECTION CIRCUIT ON I/O PINS

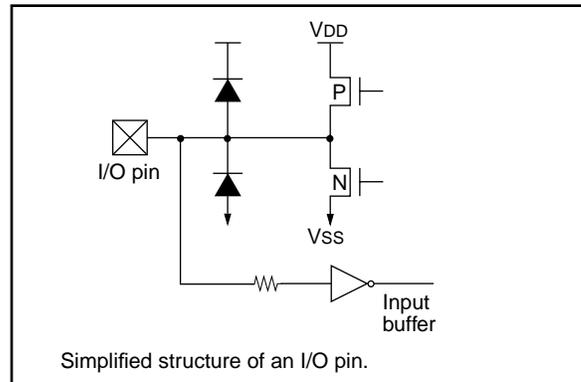


The least expensive method to limit current is to use a high value resistor. A block diagram is shown in Figure 2. The power line voltage is current limited by the resistor and then clamped by the input protection diodes internal to the PIC16C5X. A typical input waveform is shown in Figure 5. A 115 VAC, 60 cycle sine wave will traverse from 0 to 2V in 32 μ s, therefore a typical threshold of 2V on a PIC16C5X I/O port will permit zero crossing detection accuracy of about 30 μ s. If the typical capacitance on an I/O pin is 5 pF, then R should be ($t = RC$) 6 M Ω or less for best zero crossing accuracy. A 5 M Ω resistor with 115 VAC applied to it will limit current to 32 μ A, a value which is well within the safety margin of the PIC16C5X.

FIGURE 2: LIMITING CURRENT USING AN EXTERNAL RESISTOR

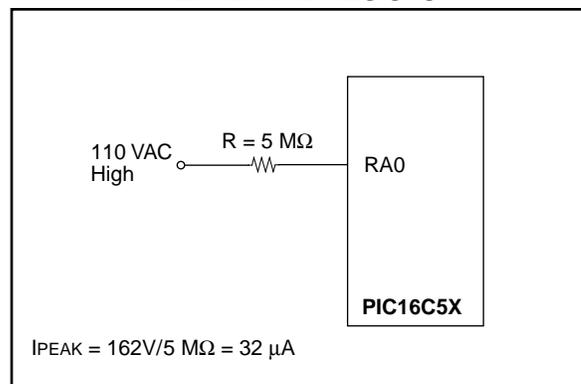

The user needs to be aware that the circuit required to connect the T0CKI input to an AC power line is slightly different than the other I/O pins. Each of the I/O pins has two diodes for input protection whereas the T0CKI pin has only one protection diode connected to V_{SS} (Figure 3). Therefore, it is necessary to connect a diode externally between the T0CKI pin and V_{DD} in order to clamp the voltage on the T0CKI pin to V_{DD} + 0.6V (approximately). See Figure 4. It is also recommended that resistor R be at least 2 M Ω .

FIGURE 3: INPUT STRUCTURE OF $\overline{\text{MCLR}}$ AND T0CKI PINS

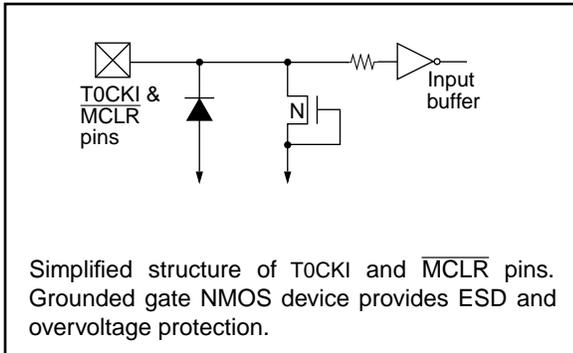

RELIABILITY

Reliability of production devices that are directly connected to AC power is always a concern. Two failure modes are possible. First, the series resistor of Figure 1 might fail short, destroying the microcontroller.

A short is the most unlikely failure mode for a resistor, and resistors are more reliable than transformers or capacitors, which are the alternate components for measuring line parameters. This reliability can be enhanced even further by using two resistors in series. Both would have to fail short to cause catastrophic failure, a very unlikely event.

The second possible failure mode is that excessive injection of current into the PIC16C5X might cause the protection diode to open. This would allow the input to go to power line peak voltage (162V) and short the input transistor gate oxide, causing device failure. The maximum continuous injection current into an I/O pin is specified at $\pm 500 \mu\text{A}$.

FIGURE 4: CONNECTING AN AC POWER LINE TO THE T0CKI PIN


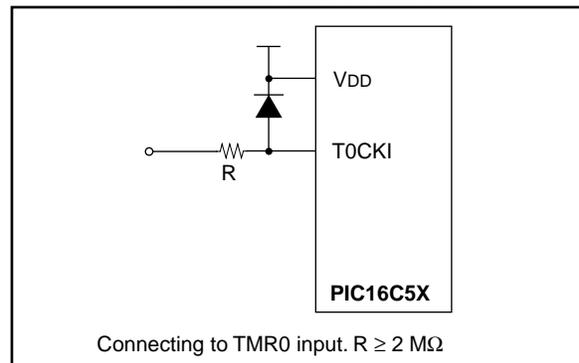


FIGURE 5: INPUT WAVEFORM

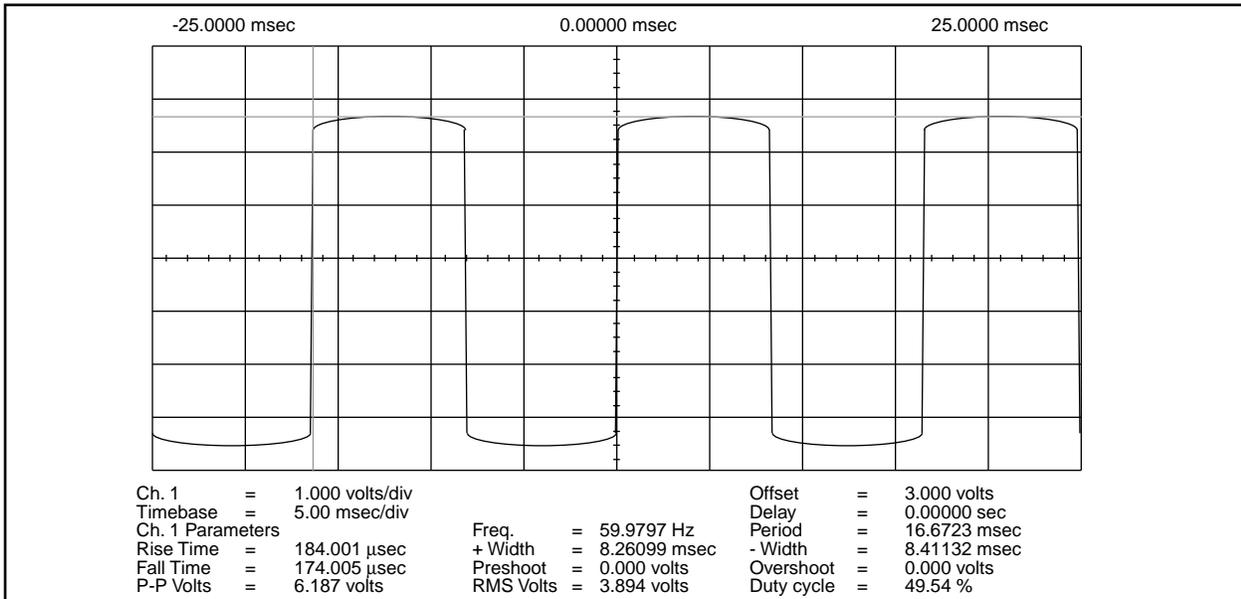

Waveform at part pin (RA0) • R = 100k; Line: 60 Hz, 110V

Note the following details of the code protection feature on PICmicro® MCUs.

- The PICmicro family meets the specifications contained in the Microchip Data Sheet.
- Microchip believes that its family of PICmicro microcontrollers is one of the most secure products of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the PICmicro microcontroller in a manner outside the operating specifications contained in the data sheet. The person doing so may be engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as “unbreakable”.
- Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our product.

If you have any further questions about this matter, please contact the local sales office nearest to you.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, FilterLab, KEELOQ, microID, MPLAB, PIC, PICmicro, PICMASTER, PICSTART, PRO MATE, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


dsPIC, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, microPort, Migratable Memory, MPASM, MPLIB, MPLINK, MPSIM, MXDEV, PICC, PICDEM, PICDEM.net, rPIC, Select Mode and Total Endurance are trademarks of Microchip Technology Incorporated in the U.S.A.

Serialized Quick Turn Programming (SQTP) is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

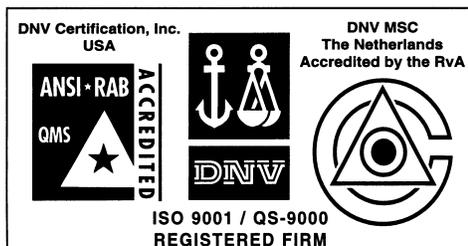

Microchip received QS-9000 quality system certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona in July 1999. The Company's quality system processes and procedures are QS-9000 compliant for its PICmicro® 8-bit MCUs, KEELOQ® code hopping devices, Serial EEPROMs and microperipheral products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001 certified.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7966 Fax: 480-792-7456

Atlanta

500 Sugar Mill Road, Suite 200B
Atlanta, GA 30350
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

New York

150 Motor Parkway, Suite 202
Hauppauge, NY 11788
Tel: 631-273-5305 Fax: 631-273-5335

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-6766200 Fax: 86-28-6766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1315, 13/F, Shenzhen Kerry Centre,
Renminnan Lu
Shenzhen 518001, China
Tel: 86-755-2350361 Fax: 86-755-2366086

Hong Kong

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaugnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471- 6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology Taiwan
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Gustav-Heinemann Ring 125
D-81739 Munich, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Arizona Microchip Technology Ltd.
505 Eskdale Road
Winnersh Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

03/01/02