

# AN10322

## Current sensing power MOSFETS

Rev. 02 — 24 June 2009

Application note

### Document information

Info	Content
<b>Keywords</b>	Current sensing, PowerMOS, senseFET, sense ratio, sense resistor, virtual earth
<b>Abstract</b>	Current sensing power MOSFETs provide an effective means of protecting automotive electronic circuits from overcurrent conditions. This application note describes the principles of operation using virtual earth current sensing and sense resistor current sensing techniques.

## Revision history

Rev	Date	Description
02	20090624	Updated to meet NXP Semiconductors house style and rewritten.
01	20040909	Initial version

## Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

## 1. Introduction

Current sensing power MOSFETs provide an effective means of protecting automotive electronic circuits from overcurrent conditions. They offer a low loss method of measuring the load current, eliminating the need for a current shunt resistor.

NXP Semiconductors has developed a range of current senseFET products to address the requirements of the automotive market as shown in [Table 1](#). All devices are based on low  $R_{DSon}$  TrenchMOS PowerMOS technology.

**Table 1. NXP senseFET range**

Device	Maximum $R_{DSon}$ (m $\Omega$ )	Sense ratio
BUK7105-40AIE	5	500:1
BUK7905-40AI	5	
BUK7C06-40AITE	6	
BUK7108-40AIE	8	
BUK7107-55AIE	7	
BUK7C08-55AITE	8	
BUK7109-75AIE	9	
BUK7C10-75AITE	10	

## 2. Principle of operation

Current senseFET technology depends on the close matching of transistor cells within the PowerMOS. A TrenchMOS device comprises many thousands of transistor cells in parallel. Elements within the device are identical and the DRAIN current is shared equally between them. The more cells that are in parallel for a given MOSFET chip area, the lower its on-state resistance will be. This principle has been the key driving force for automotive PowerMOS for many years and is well understood by both suppliers and customers.

It is possible to isolate the SOURCE connections of several cells from those of the majority and bring them out onto a separate SENSE pin. The PowerMOS can now be thought of as two transistors in parallel with a common GATE and DRAIN but separate SOURCE pins; see [Figure 1](#). When the devices are turned on, the load current will be shared as a ratio of their on-state resistances.

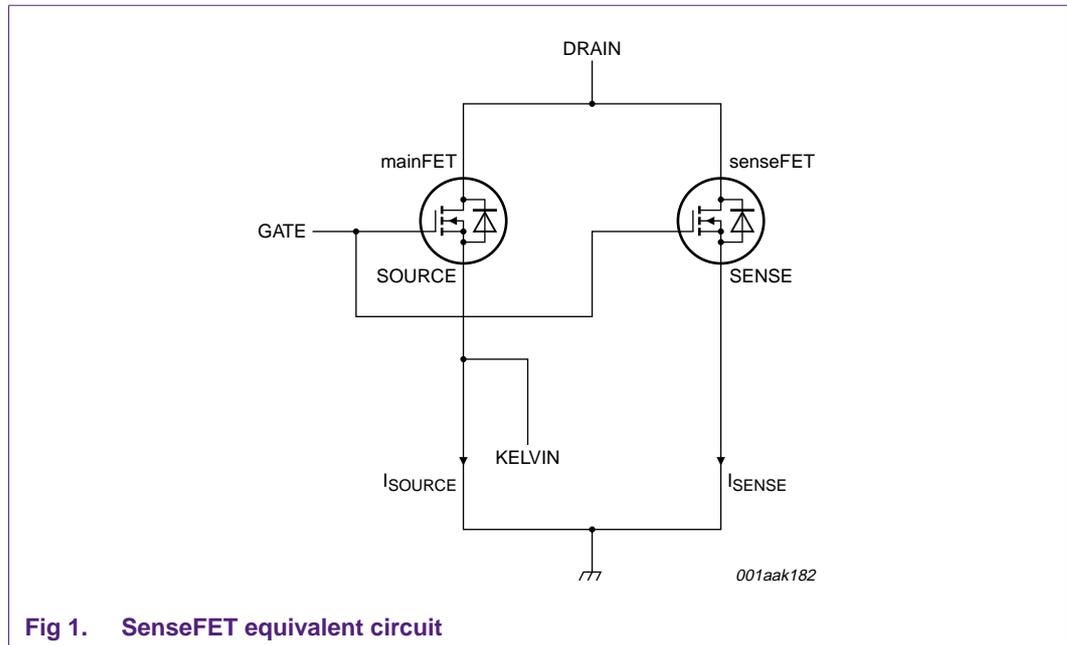


Fig 1. SenseFET equivalent circuit

The sense cells pass only a small fraction of the total load current in proportion to the ratio of their areas. This ratio is typically 500:1.

The ratio of current through the mainFET to the current through the senseFET is known as the sense ratio ( $n$ ). This ratio is defined for the condition where the SOURCE and SENSE terminals are held at the same potential. An additional KELVIN connection to the SOURCE metallization enables accurate determination of the SOURCE potential.


### 3. Virtual Earth current sensing

The virtual Earth current sensing technique gives the best performance in terms of accuracy and noise immunity over the full temperature range of the device. This method is illustrated in [Figure 2](#).


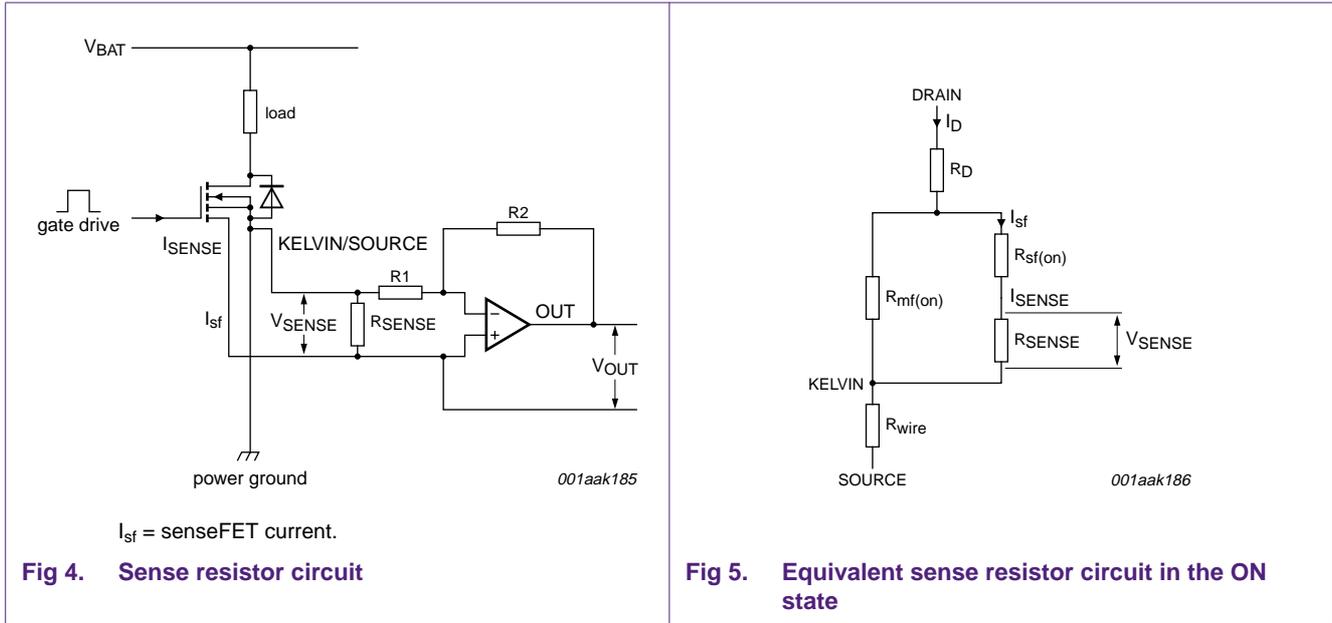
### 4. Sense resistor current sensing

The use of an external sense resistor in series with the SENSE pin offers a simpler technique for monitoring the current through the device; see [Figure 4](#) and [Figure 5](#).



In [Figure 4](#), an external operational amplifier is used to amplify the sense signal. In the equivalent circuit shown in [Figure 5](#), the resistance of the FET is separated into active and passive components, with a common DRAIN resistance. The active channels are modelled by the mainFET on-state resistance ( $R_{mf(on)}$ ) carrying the majority of the current and the senseFET on-state resistance ( $R_{sf(on)}$ ). The passive contribution from the wire resistance is denoted by  $R_{wire}$ . The circuit operates as a potential divider with design equations [Equation 2](#) and [Equation 3](#).

$$V_{out} = \left(\frac{R_2}{R_1}\right) R_{SENSE} I_{sf} \tag{2}$$

$$V_{SENSE} = I_D R_{mf(on)} \frac{R_{SENSE}}{R_{SENSE} + R_{sf(on)}} \tag{3}$$

The inclusion of  $R_{SENSE}$  increases the resistance of the mirror leg, and the sense ratio now becomes as shown in [Equation 4](#).

$$n' = n \cdot \left(1 + \frac{R_{SENSE}}{R_{sf(on)}}\right) \tag{4}$$

The maximum voltage seen on the  $I_{SENSE}$  terminal occurs when  $R_{SENSE}$  is infinite i.e. an open-circuit condition. This is known as the compliance voltage  $V_{comp}$  as shown in [Equation 5](#).

$$V_{comp} = V_{DSon} \times \left(\frac{R_{mf(on)}}{R_{mf(on)} + R_D}\right) \tag{5}$$

Therefore the mirror terminal only samples a proportion of the full DRAIN-SOURCE voltage. Fortunately, for low voltage PowerMOS the contribution from the DRAIN resistance ( $R_D$ ) is a small proportion of the total  $R_{DSon}$  and so the compliance ratio is high. This will deteriorate in higher voltage devices.


As an example, the BUK7905-40AIE  $R_{mf(on)} = 3\text{ m}\Omega$ ,  $R_{sf(on)} = 1.1\ \Omega$  and has a nominal sense ratio of 500:1. If  $R_{SENSE} = 1\ \Omega$ , when 10 A load current flows through the load this will generate  $V_{SENSE} \approx 14\text{ mV}$ . In the low side, a single rail amplifier can be used to amplify this signal to a more useful level.

The KELVIN connection to SOURCE is essential for accurate current sensing. Otherwise, voltage drops over  $R_{wire}$  that are caused by load current will add to the sense voltage and introduce a source of error. In the past this was less of an issue as a  $R_{wire}$  of 2 m $\Omega$  was only a small fraction of a 200 m $\Omega$  mainFET. But modern PowerMOS products can have on-state resistances as low as 1 m $\Omega$ , comparable with the parasitic resistances. Referencing to the KELVIN pin eliminates the wire contribution.

The main disadvantage of the sense resistor technique is that the inclusion of  $R_{SENSE}$  introduces a temperature dependence.

Imagine the case where  $R_{SENSE}$  is 0  $\Omega$ . The on-state resistance of both the mainFET and senseFET track together over temperature and the ratio of the two stays constant. In this case the current sense ratio also stays constant over temperature.


Conversely, if  $R_{SENSE}$  approaches infinity,  $V_{SENSE}$  in [Equation 3](#) now becomes  $V_{SENSE} = I_D R_{mf(on)}(T)$ , and will follow  $R_{mf(on)}$  over temperature (T). The mainFET on-state resistance almost doubles between 25 °C and 175 °C thus eroding the tolerance of the measurement. For values between the two, a balance must be struck between signal magnitude and accuracy. We normally recommend maintaining  $R_{SENSE} \ll R_{sf(on)}$  and amplifying the  $V_{SENSE}$  signal accordingly. A typical senseFET response is shown in [Figure 6](#).

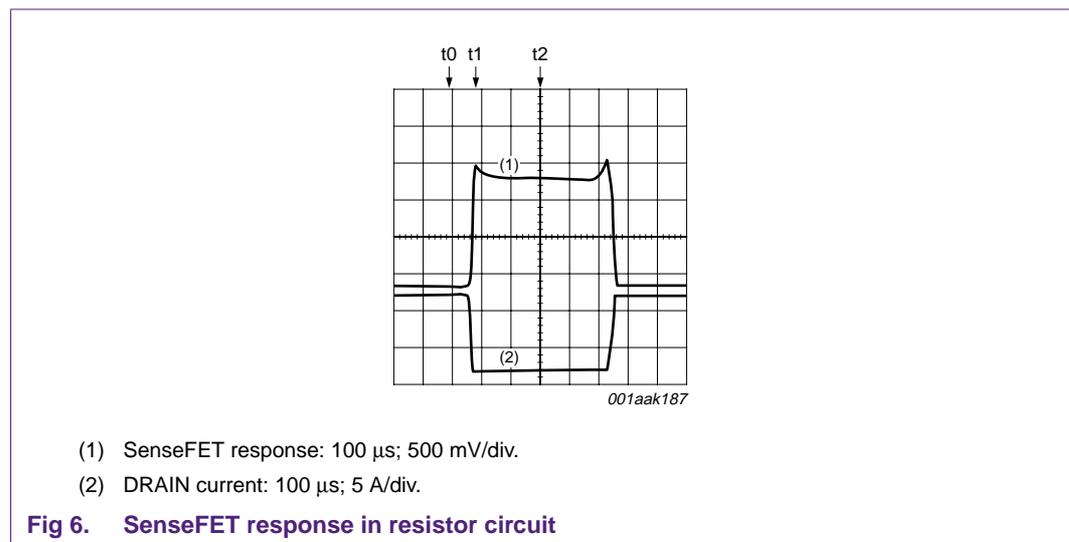

The response shown in [Figure 6](#) appears to show that the senseFET reacts instantaneously to changes in the DRAIN current, and that the sense signal contains false peaks at turn-on and turn-off. These are due to a difference in the current ratio between

the linear and the fully enhanced operating regions and are largely circuit related. This becomes more clear if we evaluate the response in terms of an effective sense ratio ( $n'$ ), which is dependent on the ratio of  $R_{SENSE}/R_{sf(on)}$  from Equation 4. Assume that  $R_{SENSE} = 1 \Omega$ .

At  $t_0$  the GATE-SOURCE voltage is zero and no current flows. Once a GATE voltage is applied, a channel forms and current begins to flow through the device, although the on-state resistance is still very high. At this point  $R_{sf(on)} \gg R_{SENSE}$  and the geometric sense ratio ( $n$ ) is measured. This yields the maximum sense signal at  $t_1$ . As the GATE is overdriven, the on-state resistance of the senseFET falls and the  $R_{SENSE}/R_{sf(on)}$  factor becomes more significant as shown in Figure 7. This continues until the final level of  $V_{GS}$  and sense ratio are reached at  $t_2$ . During turn-off, the process is reversed. Note that if  $R_{SENSE} = 0 \Omega$ , no false peaks are observed and the sense signal is similar to the virtual earth response shown in Figure 3.

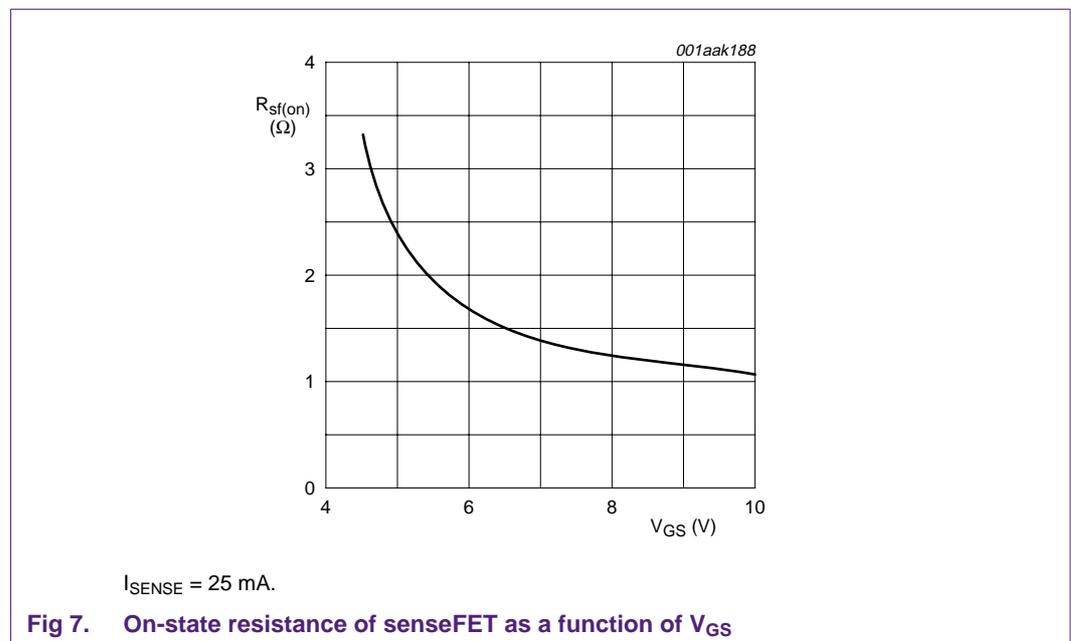

Normally, designers choose to blank out the false peaks, and to sense the current once the device is fully enhanced.

## 5. Conclusion

SenseFET devices are an effective means of protecting automotive applications. They are a low loss and cost-effective alternative to traditional current shunts whilst retaining realistic tolerances.

## 6. References

- [1] N. Zommer and J. Biran “Power current mirror devices and their applications” — Proc. Power convers. Int. Conf. June, pp275-283 (1986).

## 7. Legal information

### 7.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 7.2 Disclaimers

**General** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in medical, military, aircraft, space or life support equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from national authorities.

### 7.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

**TrenchMOS** — is a trademark of NXP B.V.

**8. Contents**

<b>1</b>	<b>Introduction</b> .....	<b>3</b>
<b>2</b>	<b>Principle of operation</b> .....	<b>3</b>
<b>3</b>	<b>Virtual Earth current sensing</b> .....	<b>4</b>
<b>4</b>	<b>Sense resistor current sensing</b> .....	<b>6</b>
<b>5</b>	<b>Conclusion</b> .....	<b>8</b>
<b>6</b>	<b>References</b> .....	<b>8</b>
<b>7</b>	<b>Legal information</b> .....	<b>9</b>
7.1	Definitions .....	9
7.2	Disclaimers .....	9
7.3	Trademarks .....	9
<b>8</b>	<b>Contents</b> .....	<b>10</b>

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.



© NXP B.V. 2009.

**All rights reserved.**

For more information, please visit: <http://www.nxp.com>  
 For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

**Date of release: 24 June 2009**  
**Document identifier: AN10322\_2**